

 


 1. Given the input waveforms shown in Figure blow, sketch the output Q_{latch} of a D latch, and output Q_{ff} of a D flip-flop



 2. The *toggle (T) flip-flop* has one input, CLK , and one output, Q . On each rising edge of CLK , Q toggles to the complement of its previous value. Draw a schematic for a T flip-flop using a D flip-flop and an inverter.



3. A JK flip-flop receives a clock and two inputs, J and K. On the rising edge of the clock, it updates the output, Q. If J and K are both 0, Q retains its old value. If only J is 1, Q becomes 1. If only K is 1, Q becomes 0. If both J and K are 1, Q becomes the opposite of its present state.

(a) Construct a JK flip-flop, using a D flip-flop and some combinational logic.

(b) Construct a D flip-flop, using a JK flip-flop and some combinational logic.

